

- ① Write Verilog code for signal assignment statement  $y = 2 * x + 3$  with 2-bit input. Show the synthesized logic symbol & gate level diagram. Write structural code in Verilog using gate level diagram.

Verilog code:

```
Module sign1(x, y);  
input [1:0] x;  
output [3:0] y;  
reg [3:0] y;  
always @ (x)  
begin  
    y = 2 * x + 3;  
end  
endmodule
```

- ⇒ The module has one input x of 2-bits and one output of 4-bits.
- ⇒ The always contains one signal 'x' in the sensitivity list. Also it has one signal assignment statement  $y = 2 * x + 3$ .
- ⇒ To synthesis the code, we construct a truth table to find the logic diagram, and use gate-level synthesis.

input(x)		output(y)			
$x_1$	$x_0$	$y_3$	$y_2$	$y_1$	$y_0$
0	0	0	0	1	1
0	1	0	1	0	1
1	0	0	1	1	1
1	1	1	0	0	1


$$y_0 = 1$$

$$y_1 = \overline{x(0)}$$


$$y_2 = \overline{x_1} x_0 + x_1 \overline{x_0} = x_1 \oplus x_0$$

$$y_3 = x_1 \cdot x_0$$

logic symbol:

 

gate level logic diagram:

 



⇒ To verify our synthesis, we write the structural code for the logic diagram (gate level)

⇒ If the simulation of structural code is same as the simulation wave form of the HDL behavioural code, then synthesis is correct.

The verilog structural code for the logic diagram:

```
module sign_struct(x,y);
```

```
input [1:0]x;
```

```
output [3:0]y;
```

```
reg [3:0]y;
```

```
always @(x)
```

```
begin
```

```
    y[0] = 1'b1;
```

```
    y[1] = ~x[0];
```

```
    y[2] = x[0] ^ x[1];
```

```
    y[3] = x[1] & x[0];
```

```
end
```

```
endmodule
```