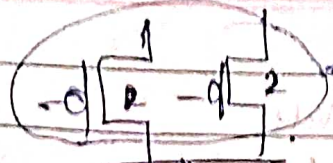


①



2 i/p NAND gate

$\overline{A \cdot B}$



series

unit cell.

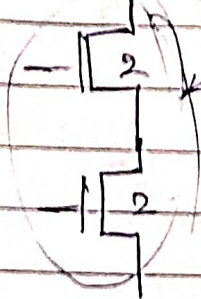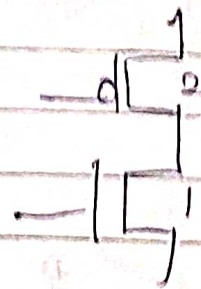

|| el.

← equivalent to 1.

pull down.

$$\left(\frac{W}{L}\right)_{eq A/B} = 1$$

$$1 = \frac{1}{\left(\frac{L}{W} + \frac{L}{W}\right)} = \frac{1}{\frac{2L}{W}}$$

$$\left(\frac{W}{L}\right) = 2$$

series  $\rightarrow$  how many series connection  $\times$  unit cell value.

$\times$  el  $\rightarrow$  each  $\times$  el connect is equivalent to unit cell.

pull down


$$\left(\frac{W}{L}\right)_{eq} = \frac{1 \times W_p \cdot inv}{1 \times 2}$$

$$\left(\frac{W}{L}\right)_{eq A/B} = 2$$






2)  $F = (A+B) \cdot (C+D)$

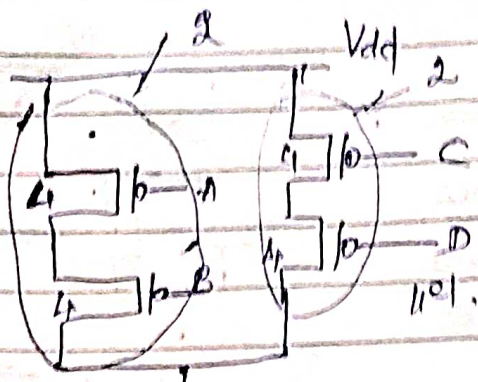

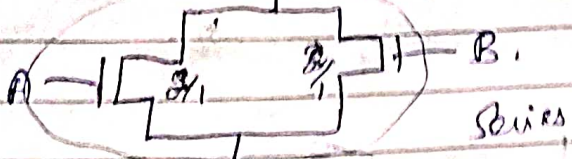NMOS  
(+) 11 el  
(-) series  
PMOS  
(+) series  
(-) 11 el



NMOS:  
 $(2 \times \frac{2}{1}) + (2 \times \frac{2}{1})$



PMOS:  
 $(2 \times \frac{1}{4}) + (2 \times \frac{1}{4})$   
 $= 1 + 1 = 2$   
 $8 + 8 = 16$

pd  $= 2 \times W_{n,inv}$   
 $(\frac{W}{L})_{eqn} = 2 \times 1 = 2$

$(\frac{W}{L})_A = (\frac{W}{L})_B = 2$   
 $(\frac{W}{L})_C = (\frac{W}{L})_D = 2$

$(\frac{W}{L})_{eqn} = \frac{1}{(\frac{1}{W}) + (\frac{1}{W})} = \frac{1}{2 \frac{1}{W}}$   
 $1 = \frac{1}{2 \frac{1}{W}} = \frac{W}{2} = 2$

another way  
for  $(\frac{W}{L})_{eqn}$ .

logical effort  
 $(Cin)_{AB} = 6$   
for  $AB = 2+4 = 6/3$

pd U

$(\frac{W}{L})_{AB} = 2$   
 $(\frac{W}{L})_{CD} = 2$

logical effort for  
 $(Cin)_{CD} = 6$   
for  $CD = 2+4 = 6/3$


$(\frac{W}{L})_p = W_{p,inv} = 2$

$2 = \frac{1}{(\frac{1}{W}) + (\frac{1}{W})} = 2 = \frac{1}{2 \frac{1}{W}}$   
 $\frac{W}{L} = 4$



③

$$F = A \cdot B + C$$

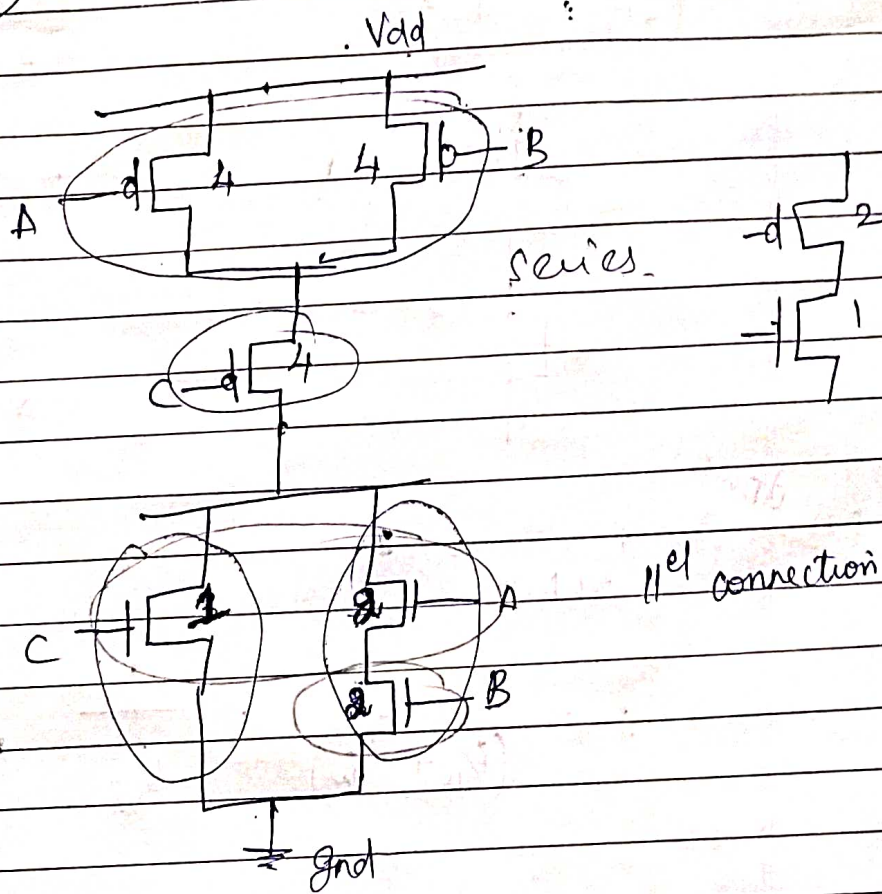

~~Pull up~~ Pull down

$$\left(\frac{W}{L}\right)_C = 1$$

$$\left(\frac{W}{L}\right)_{AB} = 1$$

~~pull~~

$$\frac{1}{\left(\frac{L}{W}\right) + \left(\frac{1}{W}\right)} = 1$$

$$\frac{1}{\frac{2L}{W}} = 1$$

$$\frac{W}{L} = 2$$

Pull up


→ series connection

$$\left(\frac{W}{L}\right)_{AB} = \left(\frac{W}{L}\right)_C = 4$$

$$\left(\frac{W}{L}\right)_{eqn} = 2 \times W_{pinV} \Rightarrow 2 \times 2 = 4$$

7

$$f = \overline{D} + A \cdot (B + C)$$

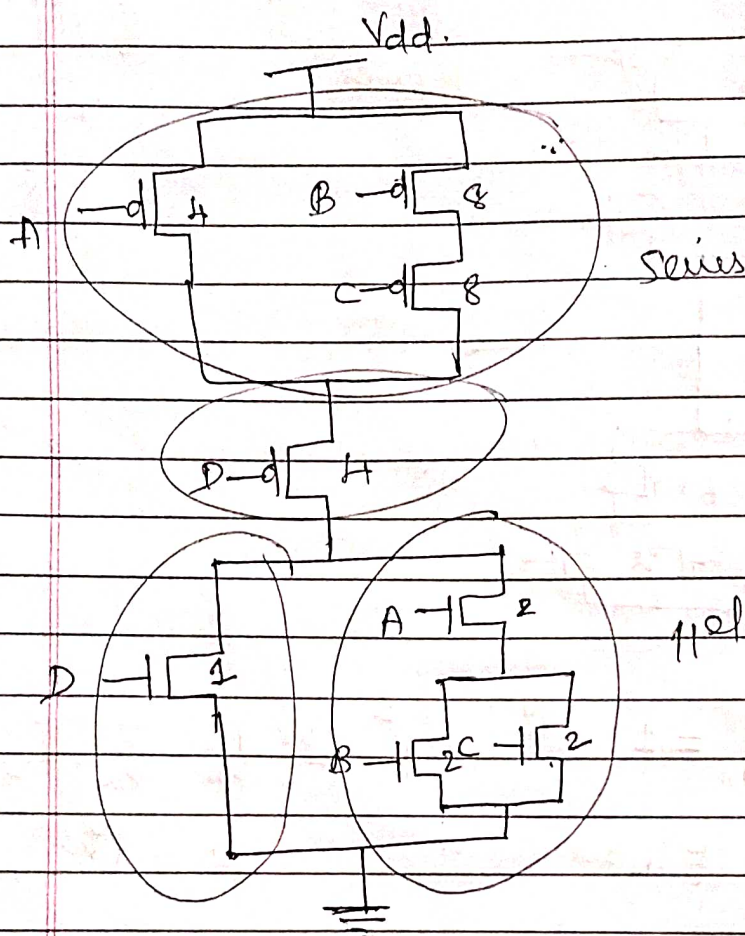

Pull down  $\left(\frac{W}{L}\right)_D = \left(\frac{W}{L}\right)_{ABC} = 1$

$$\left(\frac{W}{L}\right)_{ABC} = \frac{1}{\left(\frac{W}{L}\right)_A + \left(\frac{W}{L}\right)_{BC}} = 2 \frac{W}{L}$$

$$\left(\frac{W}{L}\right)_A = 2 \quad \left(\frac{W}{L}\right)_{BC} = 2$$

B & C  $\Rightarrow$  ||<sup>el</sup> connection

Pull up  $\left(\frac{W}{L}\right)_B = \left(\frac{W}{L}\right)_C = 2$

$2 \times 2 \Rightarrow 4$

$$\left(\frac{W}{L}\right)_{ABC} = 4 \quad \left(\frac{W}{L}\right)_D = 4$$


$$\left(\frac{W}{L}\right)_{ABC} \Rightarrow \left(\frac{W}{L}\right)_A \parallel \text{with } \left(\frac{W}{L}\right)_{BC} \quad \left(\frac{W}{L}\right)_B = 8 \quad \left(\frac{W}{L}\right)_C = 8$$

$\left(\frac{W}{L}\right)_A = 4 \quad \& \left(\frac{W}{L}\right)_{BC} = 4$



5

$$A(B+C) + DE$$

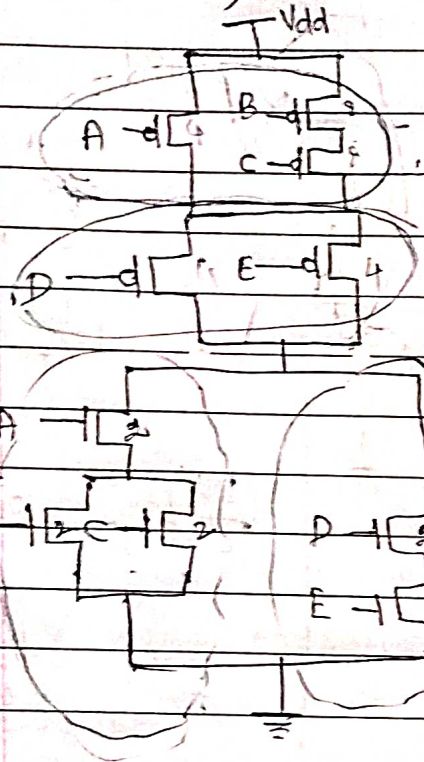

series

$$6/3 = 10/3, \frac{6}{3}$$

$$5 \times 2 = 10$$

$$9 \times 3 = 12 + 16$$

$$\frac{12}{96}$$

33

$$24$$

$$\left(\frac{W}{L}\right)_{AD} = 2 \left(\frac{W}{L}\right)_{BCDE} = 2$$

pull down

$$\left(\frac{W}{L}\right)_{ABC} = 1$$

$$\left(\frac{W}{L}\right)_{DE} = 1$$

$$\frac{9 \times 3}{6} = \frac{1}{3L} \cdot \frac{3L}{W}$$

$$1 = \frac{1}{\left(\frac{W}{L}\right)_A + \left(\frac{W}{L}\right)_{BC}}$$

$$1 = \frac{1}{\left(\frac{W}{L}\right)_A + \left(\frac{W}{L}\right)_B}$$

$$\left(\frac{W}{L}\right)$$

$$\frac{1}{\left(\frac{2L}{W}\right)} = 1$$

$$\frac{W}{L} = 2$$

$$\left(\frac{W}{L}\right)_A = 2 = \left(\frac{W}{L}\right)_{BC}$$

$$BC \rightarrow \text{parallel} \quad \left(\frac{W}{L}\right)_B = \left(\frac{W}{L}\right)_C = 2$$

pull up

PU  $\left(\frac{W}{L}\right)_{ABC}$  series  $\left(\frac{W}{L}\right)_{DE} \Rightarrow 2$  series connect


$$4 = \frac{1}{24/W} \quad 8 = \frac{W}{L}$$

$$2 \times 2 \Rightarrow 4 \Rightarrow \left(\frac{W}{L}\right)_{DE} = 4 = \left(\frac{W}{L}\right)_{ABC}$$

$$4 = \frac{1}{\frac{1}{W} + \frac{1}{W}}$$

$$\left(\frac{W}{L}\right)_D = 4 \quad \left(\frac{W}{L}\right)_E = 4 = \left(\frac{W}{L}\right)_A = \left(\frac{W}{L}\right)_{BC} = 4$$

6

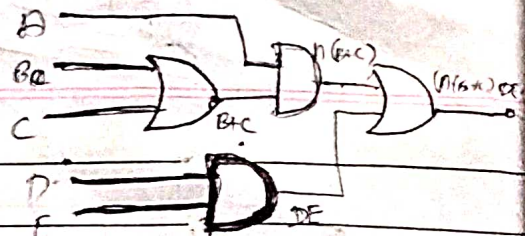




6

~~(A+B)+C~~

DATE

PAGE

$(AB+C)D$

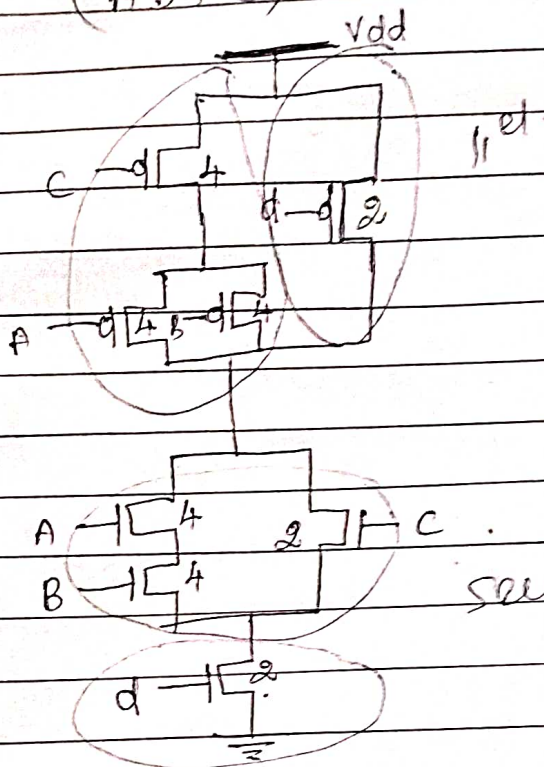

pull down  $(\frac{W}{L})_{ABC}$  series with  $(\frac{W}{L})_D$ .

$$2 \times 1 = 2$$

$$(\frac{W}{L})_D = 2 \quad (\frac{W}{L})_{ABC} = 2$$

AB are in parallel with C

$$(\frac{W}{L})_{AB} = 2 \quad (\frac{W}{L})_C = 2$$

$$2 = \frac{1}{(\frac{1}{W})_A + (\frac{1}{W})_B} = 2 = \frac{W}{2L} \Rightarrow \frac{W}{L} = 4$$

pull up  $(\frac{W}{L})_{ABC} = 2 \quad 2 (\frac{W}{L})_D = 2$

$(\frac{W}{L})_C$  is series with  $(\frac{W}{L})_{AB}$ .

$$8 = \frac{W}{L} \quad (\frac{W}{L})_C = (\frac{W}{L})_{AB} \Rightarrow 2 = \frac{1}{\frac{1}{W} + \frac{1}{W}} \Rightarrow \frac{W}{L} = 4$$

$\frac{W}{L}$   $(\frac{W}{L})_C = (\frac{W}{L})_{AB} = 4$  A & B are in parallel; so


$$(\frac{W}{L})_A = (\frac{W}{L})_B = 4$$

7

$$AB + (C + D)E$$

DATE

PAGE

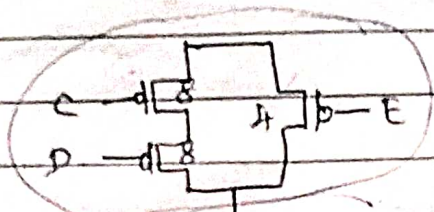

Series.


$$\frac{8 \times 2}{0} = 1$$

7

$$8 - 1$$



out

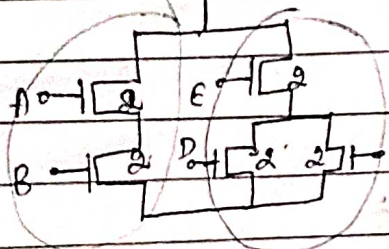

11<sup>th</sup>

Pull down

$$\left(\frac{W}{L}\right)_{AB} = 1 \quad \left(\frac{W}{L}\right)_{CD} = 1 \quad \left(\frac{W}{L}\right)_{AB} = \frac{1}{\frac{1}{W} + \frac{1}{W}}$$

$$\left(\frac{W}{L}\right)_A \text{ \& } \left(\frac{W}{L}\right)_B \text{ are series}$$

$$2 = \left(\frac{W}{L}\right)_A = \left(\frac{W}{L}\right)_B$$

$$\left(\frac{W}{L}\right)_{CD} \text{ \& } \left(\frac{W}{L}\right)_E \text{ are in series.}$$

$$\left(\frac{W}{L}\right)_{CD} = 2 \quad \left(\frac{W}{L}\right)_E = 2$$

$$C \text{ \& } D \text{ are 11<sup>th</sup> } \left(\frac{W}{L}\right)_C = \left(\frac{W}{L}\right)_D = 2$$

Pull up: 2 series connection

$$2 \times 2 = 4$$

$$\left(\frac{W}{L}\right)_{AB} = 4$$

$$\left(\frac{W}{L}\right)_{CD} = 4$$

~~CD~~ are 11<sup>th</sup> with E.

$$\left(\frac{W}{L}\right)_{CD} = 4 \quad \left(\frac{W}{L}\right)_E = 4$$


C \& D are series,

$$\left(\frac{W}{L}\right)_{CD} = 4 = \frac{1}{\frac{1}{W} + \frac{1}{W}} = 8$$

$$\left(\frac{W}{L}\right)_C = \left(\frac{W}{L}\right)_D = 8$$




# Unit CMOS Inverter:

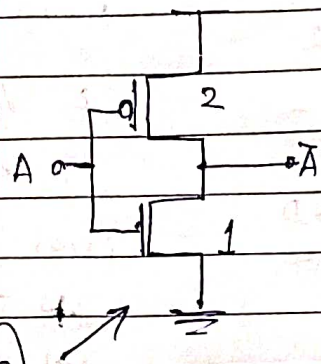

$$\left(\frac{W}{L}\right)_p = 2$$

$$\left(\frac{W}{L}\right)_n = 1$$

## NMOS

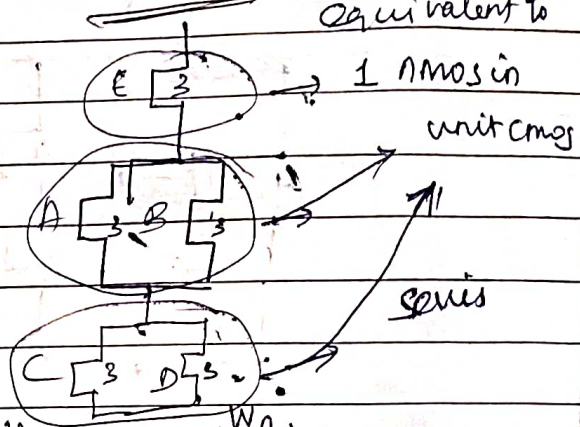

$$\left(\frac{W}{L}\right)_{eq} = 3 \times \left(\frac{W}{L}\right)_{inv} = 3 \times 1 = 3$$

$$\left(\frac{W}{L}\right)_E = 3$$

$$\left(\frac{W}{L}\right)_A = \left(\frac{W}{L}\right)_B = 3 \quad \& \quad \left(\frac{W}{L}\right)_C = \left(\frac{W}{L}\right)_D = 3$$

How many number of nmos paths are connected


don't consider about vel connection

in series

$$\left(\frac{W}{L}\right)_{eq} = \frac{1}{\left(\frac{1}{W}\right) + \left(\frac{1}{W}\right) + \left(\frac{1}{W}\right)} = \frac{1}{3 \frac{1}{W}}$$

$$1 = \frac{1}{3 \frac{1}{W}} \Rightarrow \left(\frac{W}{L}\right)_{eq} = 3$$

## PMOS

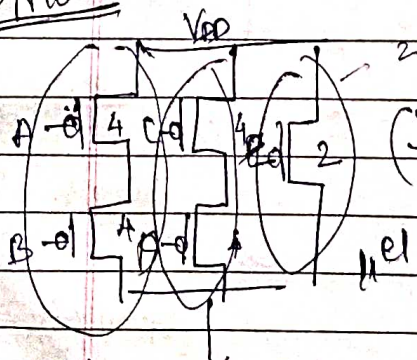


$$\left(\frac{W}{L}\right)_p = 2$$

3 path of pmos are connected in series

How many pmos paths are connected in ||.
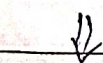
$$\left(\frac{W}{L}\right)_{eqA,B} = 2 = \left(\frac{W}{L}\right)_{eqC,D} = 2$$



$$2 = \frac{1}{\frac{1}{W} + \frac{1}{W}} = \frac{1}{2 \frac{1}{W}}$$

$$\left(\frac{W}{L}\right)_{eqE} = 2 = \frac{1}{\frac{1}{W}}$$

$$4 = \left(\frac{W}{L}\right)$$

$$\left(\frac{W}{L}\right)_A = \left(\frac{W}{L}\right)_B = 4 ; \left(\frac{W}{L}\right)_C = \left(\frac{W}{L}\right)_D = 4 ; \left(\frac{W}{L}\right)_E = 2$$




AOI 221

DATE:

PAGE:

NMOS

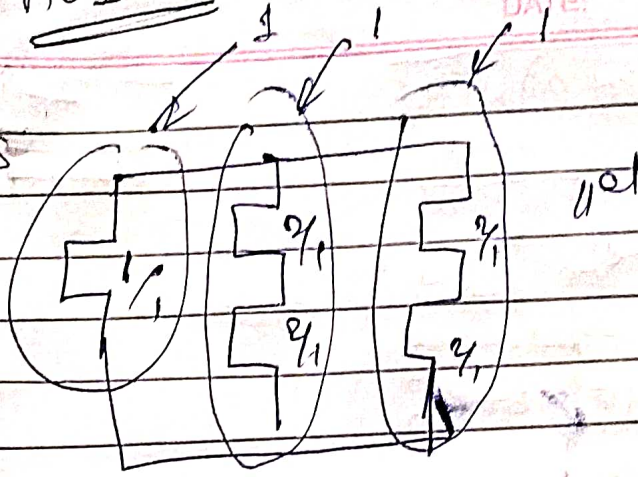

$$\left(\frac{W}{L}\right)_p = 2$$

$$\left(\frac{W}{L}\right)_n = 1$$

$$\left(\frac{W}{L}\right)_{eq A, B} = 1$$

$$\left(\frac{W}{L}\right)_{eq C, D} = 1$$

$$1 = \frac{1}{\frac{1}{2} \frac{L}{W} + \frac{1}{2} \frac{L}{W}}$$

$$1 = \frac{1}{2 \frac{L}{W}}$$


$$1 = \frac{1}{2 \frac{L}{W}}$$

$$2 = \frac{W}{L}$$

$$2 = \left(\frac{W}{L}\right) =$$

PMOS

$$\left(\frac{W}{L}\right)_E = 1$$

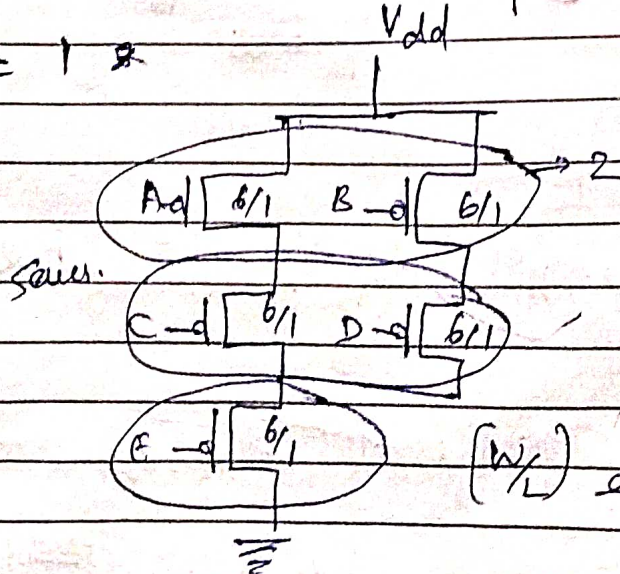

series  
3 paths.

$$\begin{aligned} \left(\frac{W}{L}\right)_{eq} &= 3 \times W_{p, inv} \\ &= 3 \times 2 \\ &= 6 \end{aligned}$$

$$\left(\frac{W}{L}\right)_{eq A, B} = \left(\frac{W}{L}\right)_{eq C, D} = \left(\frac{W}{L}\right)_E = 6$$