

# **MODULE- 2**

**ASIC Library Design:** Logical effort: predicting delay, logical area and logical efficiency, logical paths, multi stage cells, optimum delay, optimum no. of stages, library cell design. (3.3 & 3.4)

**Low-Level Design Entry:** Schematic Entry: Hierarchical design. The cell library, Names, Schematic, Icons & Symbols, Nets, schematic entry for ASIC'S, connections, vectored instances and buses, Edit in place, attributes, Netlist screener, Schematic-Entry tools Back annotation. (9.1)

by,

Dr.P.Vimala  
Department of ECE  
Dayananda Sagar College of Engineering  
Bangalore

Figures from M.J.S .Smith, - “**Application - Specific Integrated Circuits**”

# Logical Effort

- Explore a delay model- basis for time constant analysis
- All nonideal component of delay,  $t_q$ , includes
  - (1) delay due to internal parasitic capacitance;
  - (2) the time for the input to reach the switching threshold of the cell;
  - (3) the dependence of the delay on the slew rate of the input waveform.
- With these assumptions we can express the delay as follows:

$$t_{PD} = R ( C_{out} + C_p ) + t_q$$

- Logic cell by a scaling factor,  $s$ 
  - pull resistance  $R$  will decrease to  $R / s$
  - parasitic capacitance  $C_p$  will increase to  $sC_p$
  - assume that  $t_q$  scales linearly with  $s$  for all cells ( $st_q$ )

Total cell delay  $t_{PD} = ( R / s ) \cdot ( C_{out} + sC_p ) + st_q$

- Rewrite above Eq. using the input capacitance of the scaled logic cell  $C_{in} = sC$ ,

$$t_{PD} = RC \frac{C_{out}}{C_{in}} + RC_p + st_q$$

- Finally we normalize the delay using the time constant formed from the pull resistance  $R_{inv}$  and the input capacitance  $C_{inv}$  of a minimum-size inverter:  

$$d = \frac{(RC)(C_{out}/C_{in}) + RC_p + st_q}{t}$$
where,  $t = R_{inv} C_{inv}$

- The delay equation is the sum of three terms with special names as follows:  $d = f + p + q$

delay = effort delay + parasitic delay + nonideal delay

- Effort delay,  $f = gh$

where, g-logical effort ( $g = RC/t$ ) & h-electrical effort ( $h = C_{out}/C_{in}$ )

- Parasitic delay,  $p = RC_p/t$

- Nonideal delay,  $q = st_q/t$


- delay = (logical effort X electrical effort) + parasitic delay + nonideal delay

# logical effort , $g = RC / t$

- R and C will change as we scale a logic cell, but the RC product stays the same
- Logical effort is independent of the size of a logic cell
- We can find logical effort by scaling a logic cell to have the same drive as a 1X minimum-size inverter
- Then the logical effort, g, is the ratio of the input capacitance,  $C_{in}$ , of the 1X logic cell to  $C_{inv}$ .

**The logical effort of a cell ( $g$ ) =  $C_{in} / C_{inv}$**

Cell	Cell effort (logic ratio = 2)	Cell effort (logic ratio = r)	Parasitic delay/ $t$	Nonideal delay/ $t$
inverter	1 (by definition)	1 (by definition)	$p_{inv}$ (by definition) <u>1</u>	$q_{inv}$ (by definition) <sup>1</sup>
n -input NAND	$(n + 2)/3$	$(n + r)/(r + 1)$	$n p_{inv}$	$n q_{inv}$
n -input NOR	$(2n + 1)/3$	$(nr + 1)/(r + 1)$	$n p_{inv}$	$n q_{inv}$

 

- For a two-input NAND cell, the logical effort,  $g=4/3$

(a) Find the input capacitance,  $C_{inv}$ , looking into the input of a minimum-size inverter in terms of the gate capacitance of a minimum-size device

(b) Size a logic cell to have the same drive strength as a minimum-size inverter (assuming a logic ratio of 2). The input capacitance looking into one of the logic-cell terminals is then  $C_{in}$

(c) The logical effort of a cell is  $C_{in} / C_{inv}$

We can size a logic cell using these basic rules:

- Any string of transistors connected between a power supply and the output in a cell with 1X drive should have the same resistance as the n -channel transistor in a 1X inverter.
- A transistor with shape factor  $W_1 / L_1$  has a resistance proportional to  $L_1 / W_1$  (so the larger  $W_1$  is, the smaller the resistance).
- Two transistors in parallel with shape factors  $W_1 / L_1$  and  $W_2 / L_2$  are equivalent to a single transistor  $(W_1 / L_1 + W_2 / L_2) / 1$ . For example, a 2/1 in parallel with a 3/1 is a 5/1.
- Two transistors, with shape factors  $W_1 / L_2$  and  $W_2 / L_2$  , in series are equivalent to a single  $1 / (L_1 / W_1 + L_2 / W_2)$  transistor.

# Predicting Delay

Example: Let us predict the delay of a three-input NOR logic cell with 2X drive, driving a net with a fan out of four, with a total load capacitance of 0.3 pF.

Where

For C5 technology,  $C_{inv}$  is approximately 0.036 pF and  $q_{inv}=1.7$

We can calculate  $C_{in}$  from the fact that the input gate capacitance of a 1X drive, three-input NOR logic cell is equal to  $gC_{inv}$  and for a 2X logic cell,  $C_{in}=2 gC_{inv}$

The delay of the NOR logic cell, in units of  $t$ ,

For C5 technology,  $t = 0.06 ns$

$$p = 3 p_{inv} \text{ and } q = 3 q_{inv}$$

Absolute delay,  $t_{pd} = 12.3 * 0.06 ns = 0.74 ns$

$= 12.266667 t$

$$gh = g \frac{C_{out}}{C_{in}} = \frac{g \cdot (0.3 \text{ pF})}{2 g C_{inv}} = \frac{(0.3 \text{ pF})}{(2) \cdot (0.036 \text{ pF})}$$

$$d = gh + p + q = \frac{0.3 \times 10^{12}}{(2) \cdot (0.036 \times 10^{12})} + (3) \cdot (1) + (3) \cdot (1.7)$$

In the C5 library,

- The delay for a 2X drive, three-input NOR logic cell is  $t_{PD} = (0.03 + 0.72C_{out} + 0.60)$  ns
- With  $C_{out}=0.3\text{pF}$ ,  $t_{PD} = 0.03 + (0.72) \cdot (0.3) + 0.60 = \mathbf{0.846\text{ ns}}$  compared to our prediction of **0.74ns**


Error comes here due to,

- Inaccuracy in predicting the nonideal delay
- Logical effort gives us a method to examine relative delays and not accurately calculate absolute delays.
- More important is that logical effort gives us an insight into why logic has the delay.



# Logical Area and Logical Efficiency


## Example -1 (OAI221)

 

An **OAI221** logic cell

- Logical-effort vector  $g=(7/3, 7/3, 5/3)$
- The logical area is 33 logical squares

## Example -2 (AOI221)

 

An **AOI221** logic cell

- $g=(8/3, 8/3, 7/3)$
- Logical area is 39 logical squares
- Less logically efficient than OAI221